

CS64 Week 6 Lecture 1

Kyle Dewey

Overview

- Tail call optimization
- Introduction to circuits
- Digital design: single bit adders
- Circuit minimization
 - Boolean algebra
 - Karnaugh maps
 - Exploiting *don't cares*

More Recursion

- What's special about the following recursive function?

```
int recFac(int n, int accum) {  
    if (n == 0) {  
        return accum;  
    } else {  
        return recFac(n - 1, n * accum);  
    }  
}
```

More Recursion

- What's special about the following recursive function?
 - It is *tail recursive* - with the right optimization, uses constant stack space
 - We can do this in assembly -
`tail_recursive_factorial.asm`

```
int recFac(int n, int accum) {  
    if (n == 0) {  
        return accum;  
    } else {  
        return recFac(n - 1, n * accum);  
    }  
}
```

Dispelling the Magic: Circuits

Why Binary?

- Very convenient for a circuit
 - Two possible states: on and off
 - 0 and 1 correspond to on and off

Relationship to Bitwise Operations

- You're already familiar with bitwise OR, AND, XOR, and NOT
- These same operations are fundamental to circuits
 - Basic building blocks for more complex things

Single Bits

- For the moment, we will deal only with individual bits
- Later, we'll see this isn't actually that restrictive

Operations on Single Bits: AND





Operations on Single Bits: OR



Operations on Single Bits: XOR



Operations on Single Bits: NOT

  


Recall: Addition


Addition with Single Bits

$\begin{array}{r} 0 \\ 0 \\ +0 \\ \hline 0 \end{array}$	$\begin{array}{r} 0 \\ 0 \\ +1 \\ \hline 1 \end{array}$	$\begin{array}{r} 0 \\ 1 \\ +0 \\ \hline 1 \end{array}$	$\begin{array}{r} 0 \\ 1 \\ +1 \\ \hline 0 \end{array} \text{ Carry: 1}$
$\begin{array}{r} 1 \\ 0 \\ +0 \\ \hline 1 \end{array}$	$\begin{array}{r} 1 \\ 0 \\ +1 \\ \hline 0 \end{array} \text{ Carry: 1}$	$\begin{array}{r} 1 \\ 1 \\ +0 \\ \hline 0 \end{array} \text{ Carry: 1}$	$\begin{array}{r} 1 \\ 1 \\ +1 \\ \hline 1 \end{array} \text{ Carry: 1}$


In Summary

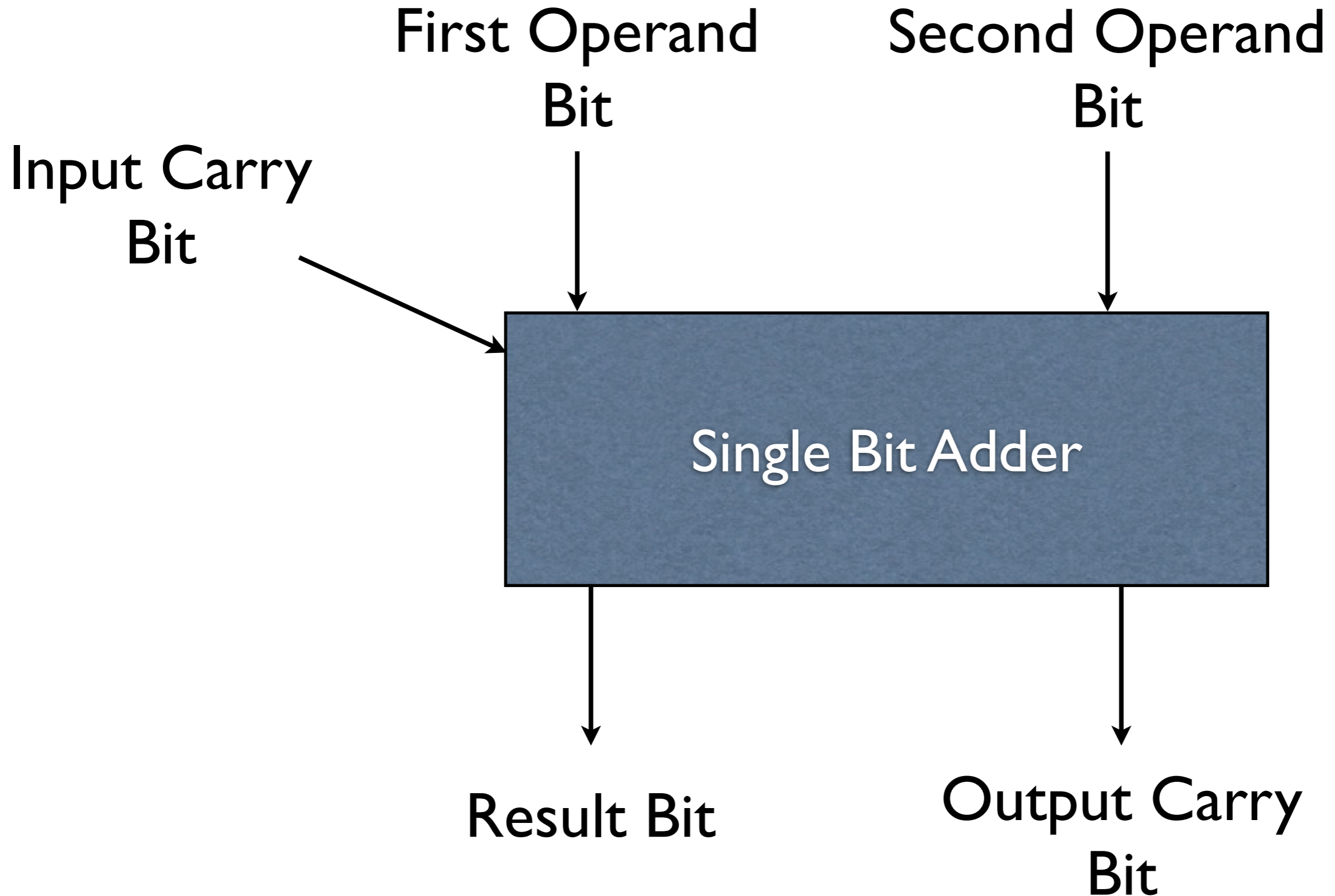

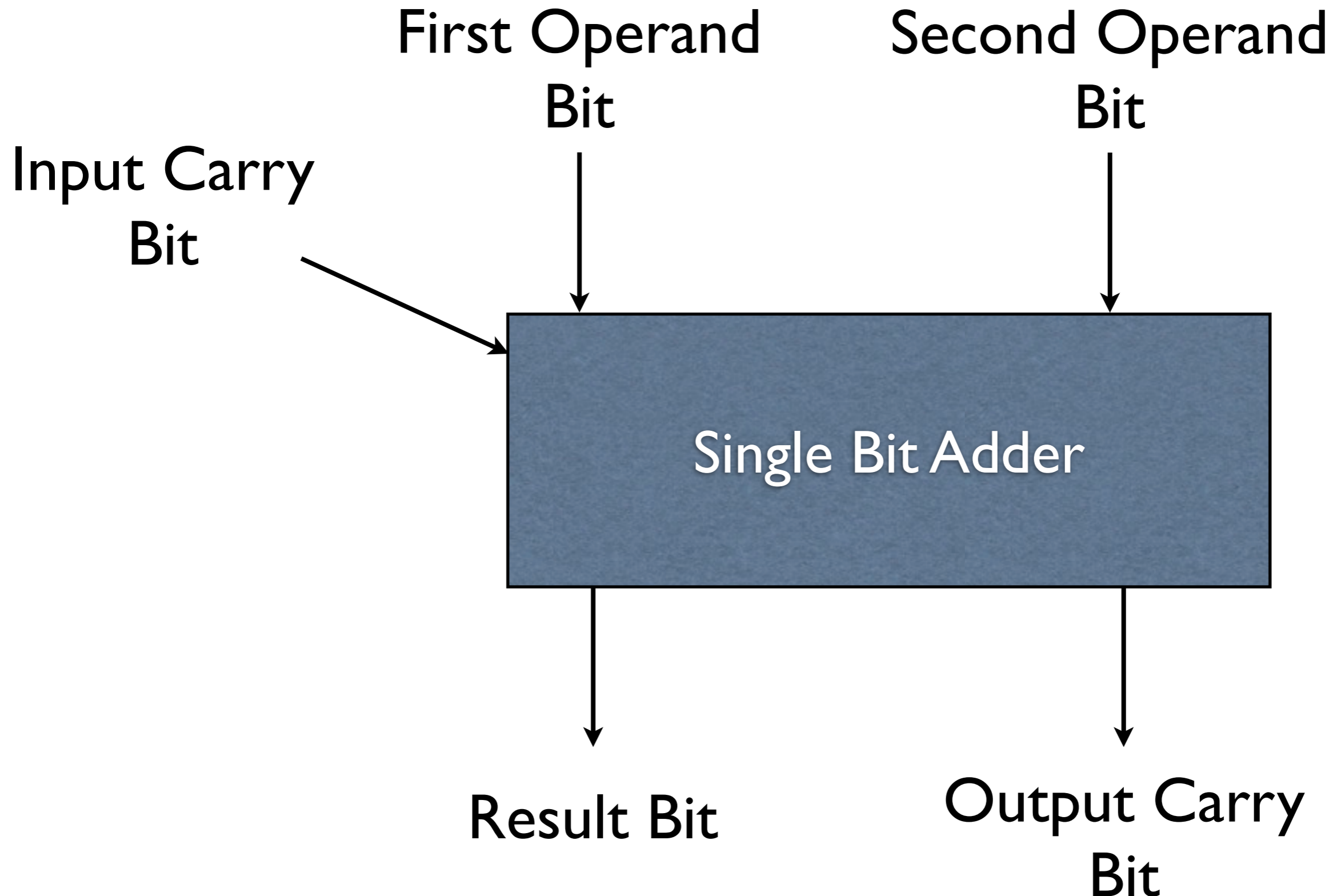
- How can we adapt this to add multi-digit binary numbers together?




Putting it Together

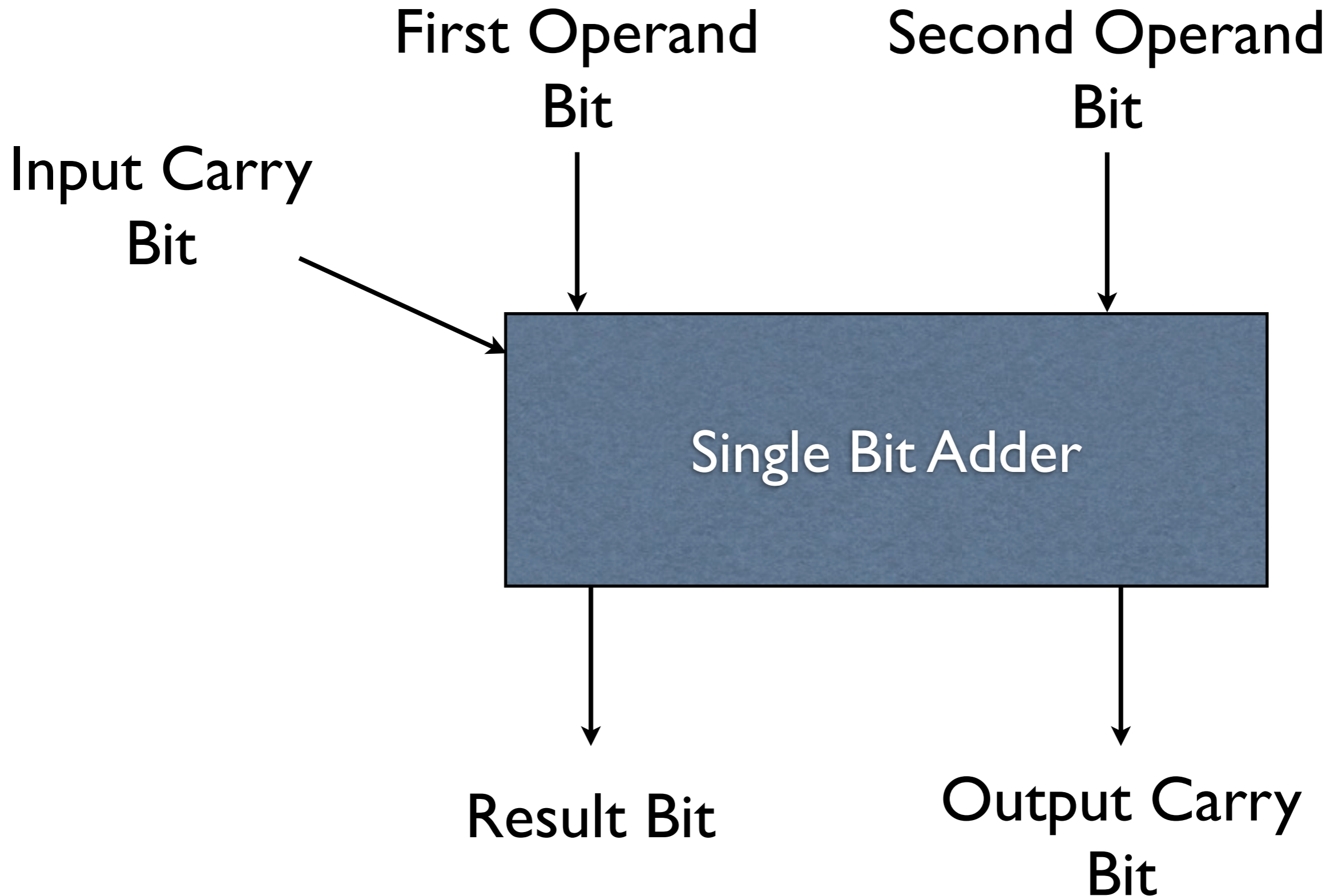

Putting it Together

 










Recall: Single Bit Adders

 


Stringing them Together

 For two three-bit numbers, A and B , resulting in a three-bit result R



 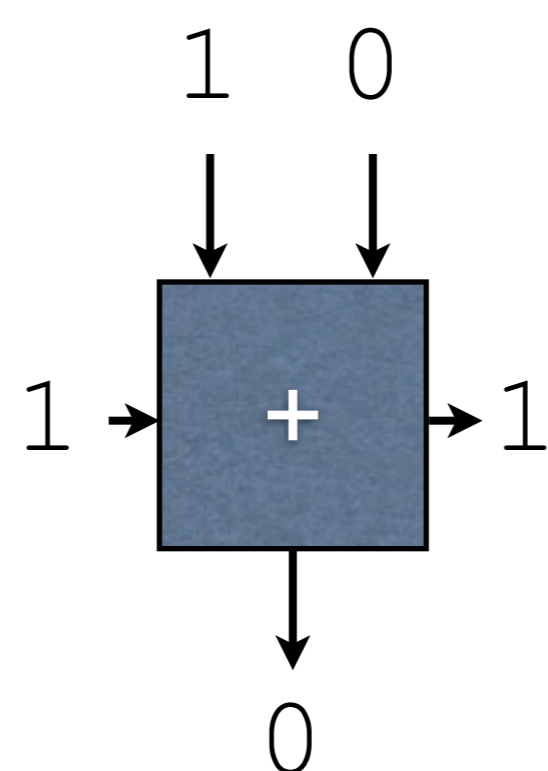      


As a Truth Table

 

C_I	I_1	I_2	C_O	R
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

As a Truth Table

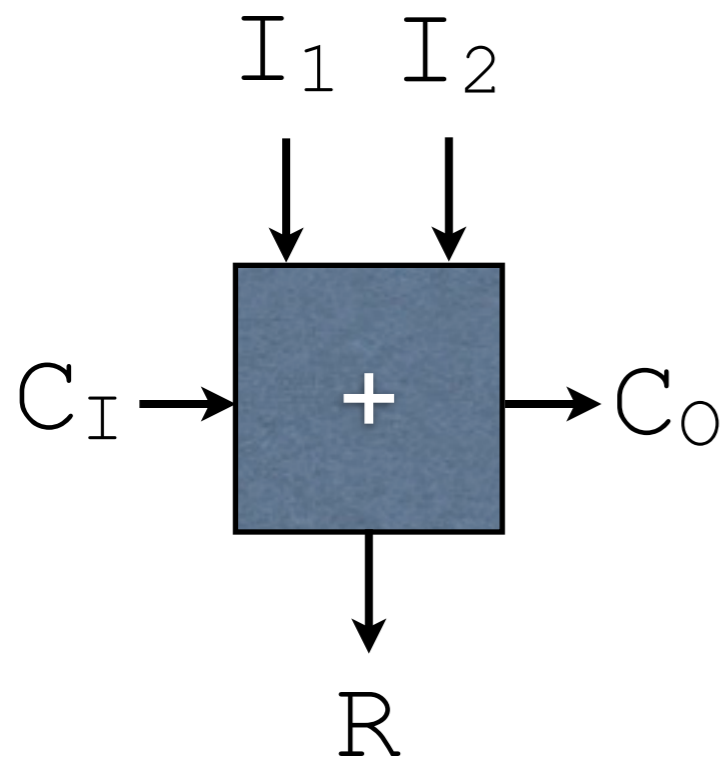Question: how can this be turned into a circuit?



C_I	I_1	I_2	C_O	R
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Sum of Products

- Variables: $A, B, C...$
- Negation of a variable: $\bar{A}, \bar{B}, \bar{C}...$

Sum of Products

- Another way to look at OR: sum (+)

$$A + B$$

- Another way to look at AND: multiplication (*)

$$A * B$$

$$AB$$

Sum of Products Example

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

Sum of Products Example

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

Sum of Products

Example

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

$$O = \bar{A} * B$$

Sum of Products

Example

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

$$O = \bar{A} * B + A * \bar{B}$$

Sum of Products

C_I	I_1	I_2	C_O	R
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Question: What would the sum of products look like for this table?
(Note: need one equation for each output.)

Sum of Products

C_I	I_1	I_2	C_O	R
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Question: What would the sum of products look like for this table?
(Note: need one equation for each output.)

Answer in the presenter notes.

In-Class Example: Shift Left by 1

Circuit Minimization

Motivation

- Unnecessarily large programs: bad
- Unnecessarily large circuits: Very Bad™
 - Why?

Motivation

- Unnecessarily large programs: bad
- Unnecessarily large circuits: Very Bad™
 - Why?
 - Bigger circuits = bigger chips = higher cost (non-linear too!)
 - Longer circuits = more time needed to move electrons through = slower

Simplification

- Real-world formulas can often be simplified, according to algebraic rules
 - How might we simplify the following?

$$R = A * B + !A * B$$

Simplification

- Real-world formulas can often be simplified, according to algebraic rules
 - How might we simplify the following?

$$R = A * B + !A * B$$

$$R = B (A + !A)$$

$$R = B (\text{true})$$

$$R = B$$

Simplification Trick

- Look for products that differ only in one variable
 - One product has the original variable (A)
 - The other product has the other variable ($\neg A$)

$$R = A * B + \neg A * B$$

Additional Example 1

$!ABCD + ABCD + !AB!CD + AB!CD$

Additional Example 1

$\overline{A}BCD + ABCD + \overline{A}B\overline{C}D + AB\overline{C}D$

$BCD(A + \overline{A}) + \overline{A}B\overline{C}D + AB\overline{C}D$

Additional Example 1

$\overline{A}BCD + ABCD + \overline{A}B\overline{C}D + AB\overline{C}D$

$BCD(A + \overline{A}) + \overline{A}B\overline{C}D + AB\overline{C}D$

$BCD + \overline{A}B\overline{C}D + AB\overline{C}D$

Additional Example 1

$$\overline{A}BCD + ABCD + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD(A + \overline{A}) + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD + B\overline{C}D(\overline{A} + A)$$

Additional Example 1

$$\overline{A}BCD + ABCD + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD(A + \overline{A}) + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD + B\overline{C}D(\overline{A} + A)$$
$$BCD + B\overline{C}D$$

Additional Example 1

$$\overline{A}BCD + ABCD + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD(A + \overline{A}) + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD + B\overline{C}D(\overline{A} + A)$$
$$BCD + B\overline{C}D$$
$$BD(C + \overline{C})$$

Additional Example 1

$$\overline{A}BCD + ABCD + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD(A + \overline{A}) + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD + B\overline{C}D(\overline{A} + A)$$
$$BCD + B\overline{C}D$$
$$BD(C + \overline{C})$$

BD

Additional Example 2

$!A!BC + A!B!C + !ABC + !AB!C + A!BC$

Additional Example 2

$!A!BC + A!B!C + !ABC + !AB!C + A!BC$

$!A!BC + A!BC + A!B!C + !ABC + !AB!C$

Additional Example 2

$!A!BC + A!B!C + !ABC + !AB!C + A!BC$

$!A!BC + A!BC + A!B!C + !ABC + !AB!C$

$!BC(A + !A) + A!B!C + !ABC + !AB!C$

Additional Example 2

$\!A\!BC + A\!B\!C + \!ABC + \!AB\!C + A\!BC$

$\!A\!BC + A\!BC + A\!B\!C + \!ABC + \!AB\!C$

$\!BC(A + \!A) + A\!B\!C + \!ABC + \!AB\!C$

$\!BC + A\!B\!C + \!ABC + \!AB\!C$

Additional Example 2

$$!A!BC + A!B!C + !ABC + !AB!C + A!BC$$

$$!A!BC + A!BC + A!B!C + !ABC + !AB!C$$

$$!BC(A + !A) + A!B!C + !ABC + !AB!C$$

$$!BC + A!B!C + !ABC + !AB!C$$

$$!BC + A!B!C + !AB(C + !C)$$

Additional Example 2

$!A!BC + A!B!C + !ABC + !AB!C + A!BC$

$!A!BC + A!BC + A!B!C + !ABC + !AB!C$

$!BC(A + !A) + A!B!C + !ABC + !AB!C$

$!BC + A!B!C + !ABC + !AB!C$

$!BC + A!B!C + !AB(C + !C)$

$!BC + A!B!C + !AB$

Scaling Up

- Performing this sort of algebraic manipulation by hand can be tricky
- We can use *Karnaugh maps* to make it immediately apparent as to what can be simplified

Example

$$R = A * B + !A * B$$

Example


$$R = A * B + !A * B$$

A	B	O
0	0	0
0	1	1
1	0	0
1	1	1

Example

$$R = A * B + !A * B$$


A	B	O
0	0	0
0	1	1
1	0	0
1	1	1

 

Example

$$R = A * B + !A * B$$


A	B	O
0	0	0
0	1	1
1	0	0
1	1	1

 

Example

$$R = A * B + !A * B$$

A	B	O
0	0	0
0	1	1
1	0	0
1	1	1

 


Example

$$R = A * B + !A * B$$


A	B	O
0	0	0
0	1	1
1	0	0
1	1	1

$$R = B$$

 

Three Variables

 - We can scale this up to three variables, by combining two variables on one axis
- The combined axis must be arranged such that only one bit changes per position



Three Variable Example


$$R = !A!BC + !ABC + A!BC + ABC$$

$$R = \neg A \neg B C + \neg A B C + A \neg B C + A B C$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


$$R = \neg A \neg B C + \neg A B C + A \neg B C + A B C$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 

$$R = \neg A \neg B C + \neg A B C + A \neg B C + A B C$$


A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 

$$R = \neg A \neg B C + \neg A B C + A \neg B C + A B C$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$R = C$$

 

Another Three Variable Example


$$R = !A!B!C + !A!BC + !ABC + \\ !AB!C + A!B!C + AB!C$$

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0


$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 


$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 


$$R = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C}$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

$$R = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C}$$


A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$$R = !A + !C$$

 


Four Variable Example

$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$

$$R = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}BC\overline{D} + \overline{A}BCD + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D + A\overline{B}C\overline{D}$$


		CD			
		00	01	11	10
AB	00	1	1	0	1
	01	0	0	0	1
	11	0	0	0	0
	10	1	1	0	1
 
$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$




$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$

$$R = !B!C$$

 

$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$

$$R = !B!C + !B!D$$

 

$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$

$$R = !B!C + !B!D + !AC!D$$

		CD			
		00	01	11	10
AB	00	1	1	0	1
	01	0	0	0	1
	11	0	0	0	0
	10	1	1	0	1

K-Map Rules in Summary (I)

- Groups can contain only 1s
- Only 1s in adjacent groups are allowed (no diagonals)
- The number of 1s in a group must be a power of two (1, 2, 4, 8...)
- The groups must be as large as legally possible

K-Map Rules in Summary (2)

- All 1s must belong to a group, even if it's a group of one element
- Overlapping groups are permitted
- Wrapping around the map is permitted
- Use the fewest number of groups possible

Revisiting Problem

$$!A!BC + A!B!C + !ABC + !AB!C + A!BC$$

Revisiting Problem

$$R = \neg A \neg B C + A \neg B \neg C + \neg A B C + \neg A B \neg C + A \neg B C$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Revisiting Problem

$$R = \bar{A}\bar{B}C + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0


		BC			
A		00	01	11	10
0	0	0	1	1	1
1	1	1	1	0	0

Revisiting Problem

$$R = \neg A \neg B C + A \neg B \neg C + \neg A B C + \neg A B \neg C + A \neg B C$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$R = \neg A C$$

 


Revisiting Problem

$$R = !A!BC + A!B!C + !ABC + !AB!C + A!BC$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$R = !AC + A!B$$

 


Revisiting Problem

$$R = !A!BC + A!B!C + !ABC + !AB!C + A!BC$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$R = !AC + A!B + !AB!C$$

 

Difference

- Algebraic solution: $\bar{B}C + A\bar{B}\bar{C} + \bar{A}B$
- K-map solution: $\bar{A}C + A\bar{B} + \bar{A}B\bar{C}$
- Question: why might these differ?

Difference

- Algebraic solution: $\bar{B}C + A\bar{B}\bar{C} + \bar{A}B$
- K-map solution: $\bar{A}C + A\bar{B} + \bar{A}B\bar{C}$
- Question: why might these differ?
 - Both are *minimal*, in that they have the fewest number of products possible
 - Can be multiple minimal solutions

Difference

- Algebraic solution: $\bar{B}C + A\bar{B}\bar{C} + \bar{A}B$
- K-map solution: $\bar{A}C + A\bar{B} + \bar{A}B\bar{C}$
- Question: why might these differ?
 - Both are *minimal*, in that they have the fewest number of products possible
 - Can be multiple minimal solutions

Difference

Algebraic solution: $\neg BC + A\neg B\neg C + \neg AB$

K-map solution: $\neg AC + A\neg B + \neg AB\neg C$

		BC			
		00	01	11	10
A	0	0	1	1	1
	1	1	1	0	0

Difference

Algebraic solution: $\neg BC + A\neg B\neg C + \neg AB$

K-map solution: $\neg BC + A\neg B\neg C + \neg AB$

		BC			
		00	01	11	10
A	0	0	1	1	1
	1	1	1	0	0

Exploiting *Don't Cares* in K-Maps

Don't Cares

- Occasionally, a circuit's output will be unspecified on a given input
 - Occurs when an input's value is invalid
- In these situations, we say the output is a *don't care*, marked as an \times in a truth table

Example: Binary Coded Decimal

- Occasionally, it is convenient to represent decimal numbers directly in binary, using 4-bits per decimal digit
 - For example, a digital display



Example: Binary Coded Decimal

- Not all binary values map to decimal digits

Binary	Decimal
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7

Binary	Decimal
1000	8
1001	9
1010	X
1011	X
1100	X
1101	X
1110	X
1111	X

Significance

- Recall that in a K-map, we can only group 1s
- Because the value of a *don't care* is irrelevant, we can treat it as a 1 if it is convenient to do so (or a 0 if that would be more convenient)

Example

- A circuit that calculates if the binary coded decimal input $\% 2 == 0$

Example

- A circuit that calculates if the binary coded decimal input $\% 2 == 0$

I_3	I_2	I_1	I_0	R
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0

I_3	I_2	I_1	I_0	R
1	0	0	0	1
1	0	0	1	0
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

Example

As a K-map

		$I_1 I_0$			
		00	01	11	10
$I_3 I_2$	00	1	0	1	0
	01	1	0	1	0
	11	X	X	X	X
	10	1	0	X	X

Example

If we don't exploit *don't cares*...

		$I_1 I_0$			
		00	01	11	10
$I_3 I_2$	00	1	0	1	0
	01	1	0	1	0
	11	X	X	X	X
	10	1	0	X	X

Example

If we **do** exploit *don't cares*...

		$I_1 I_0$			
		00	01		
$I_3 I_2$	00	1	0	1	0
	01	1	0	1	0
	11	X	X	X	X
	10	1	0	X	X

Example

If we **do** exploit *don't cares*...

$$R = !I_1!I_0 + I_1I_0$$

		I_1I_0			
		00	01	11	10
I_3I_2	00	1	0	1	0
	01	1	0	1	0
	11	X	X	X	X
	10	1	0	X	X